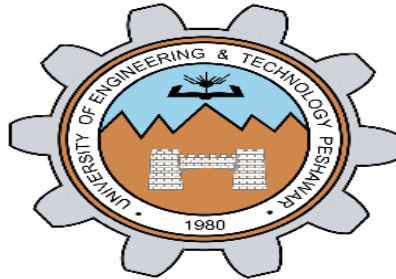


LAB REPORT NO 9



Spring 2020

CS-II lab

Submitted by: **Muhammad Ali**
Registration No: **19PWCSE1801**
Class Section: A

Submitted to:
Engr. Faiz ullah
Date:(15, 02, 2021)

Department of Computer Systems Engineering University
of Engineering and Technology, Peshawar

Lab 9

INTEGRATOR USING IC741 OP-AMP

Objective

To study the operation of the Integrator using op-amp and trace the output wave forms for sine and square wave inputs.

THEORY:

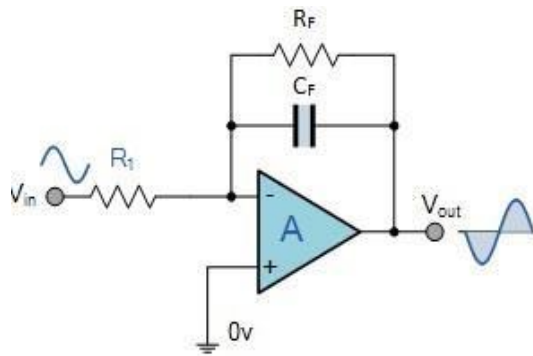


Figure 1

A circuit in which the output voltage is the integration of the input voltage is called an integrator.

$$V_o = -\frac{1}{R_1 C_F} \int V_{in} dt$$

In the practical integrator shown in Figure 1, to reduce the error voltage at the output, a resistor R_F is connected across the feedback capacitor C_F . Thus, R_F limits the low-frequency gain and hence minimizes the variations in the output voltage.

Integrator has wide applications in

1. Analog computers used for solving differential equations in simulation arrangements.
2. A/D Converters.
3. Signal wave shaping.
4. Function Generators.

Equipment:

1. Oscilloscope

2. AC Function Generator
3. Digital Multimeter

Components:

1. Resistors: $10k\Omega$, $22k\Omega$
2. Capacitor $0.1\mu F$
3. Op-amp 741

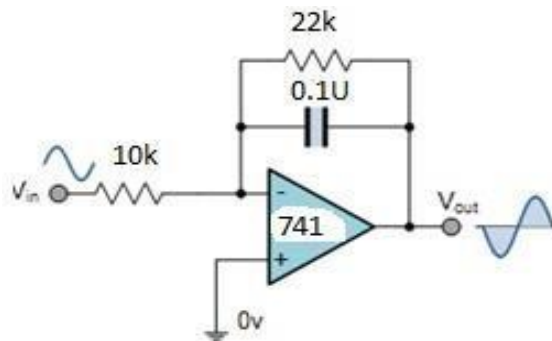


Figure 2

PROCEDURE:

1. Connect the components/equipment as shown in the circuit diagram Figure 2.
2. Switch ON the power supply.
3. Apply sine wave at the input terminals of the circuit using function Generator.
4. Connect channel-1 of CRO at the input terminals and channel-2 at the output terminals.
5. Observe the output of the circuit on the CRO which is a cosine wave (90° phase shifted from the sine wave input) and note down the position, the amplitude and the time period of V_{in} & V_o .
6. Now apply the square wave as input signal.
7. Observe the output of the circuit on the CRO which is a triangular wave and note down the position, the amplitude and the time period of V_{in} & V_o .
8. Plot the output voltages corresponding to sine and square wave inputs as shown in the Figure 3 below.


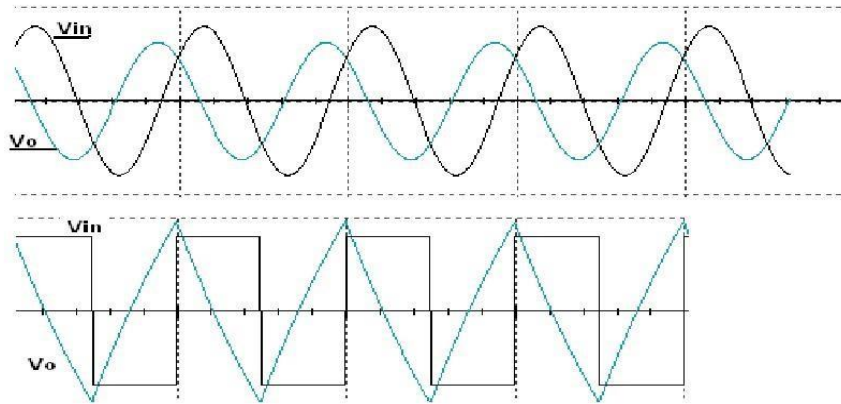


Figure 3


Data Table:

$V_{in(p-p)}$	Frequency	V_o (Theoretical)	V_o (Experimental)	%Error
1V	1kHz	$0.1592\cos 2\pi 1kHz t$	$0.150\cos 2\pi 1kHz t$	5%
2V	1kHz	$0.31\cos 2\pi 1kHz t$	$0.34\cos 2\pi 1kHz t$	9%
1V	2kHz	$0.07\cos 2\pi 2kHz t$	$0.08\cos 2\pi 2kHz t$	12%
2V	1.5kHz	$0.21\cos 2\pi 1.5kHz t$	$0.20\cos 2\pi 1.5kHz t$	4%
2.5V	2.5kHz	$0.15\cos 2\pi 2.5kHz t$	$0.16\cos 2\pi 2.5kHz t$	6%


For $V_0=1$, $f=1\text{kHz}$: -

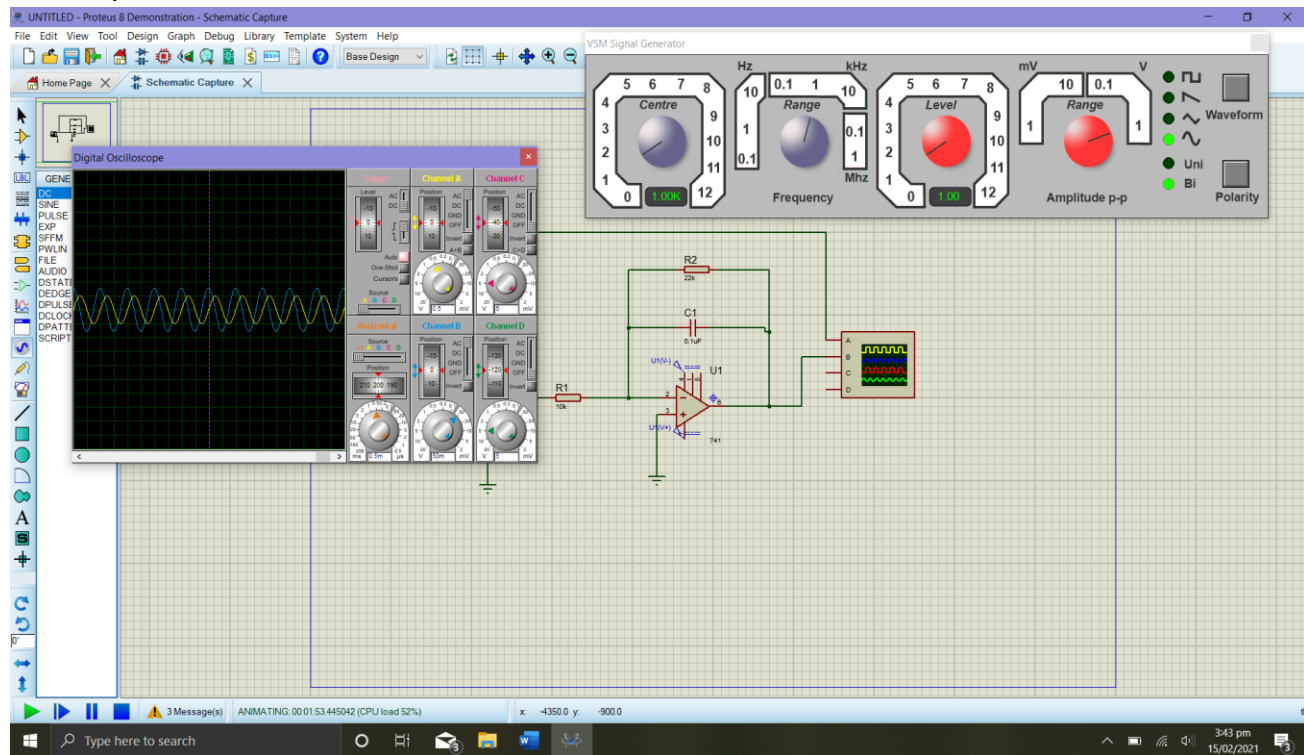

For $V_0=1$, $f=2\text{kHz}$: -

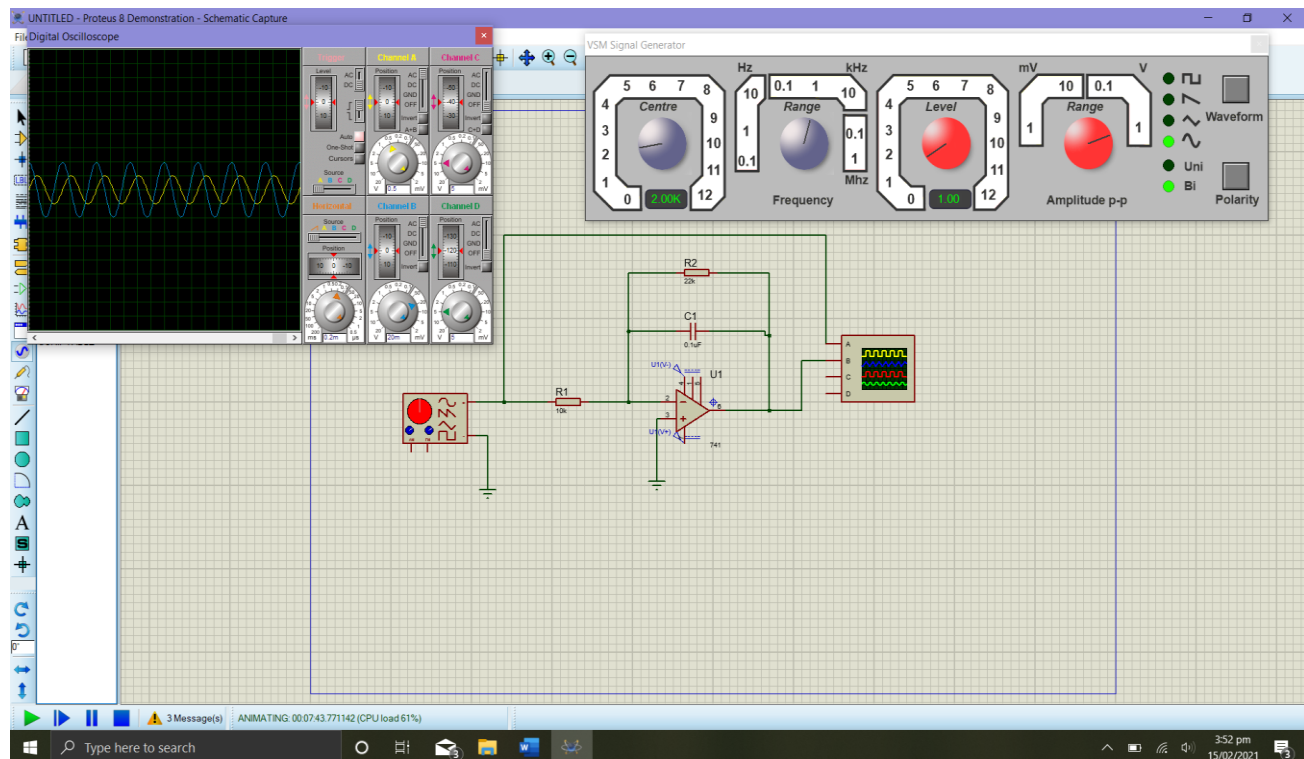

For $V_0=2$, $f=1.5\text{kHz}$: -

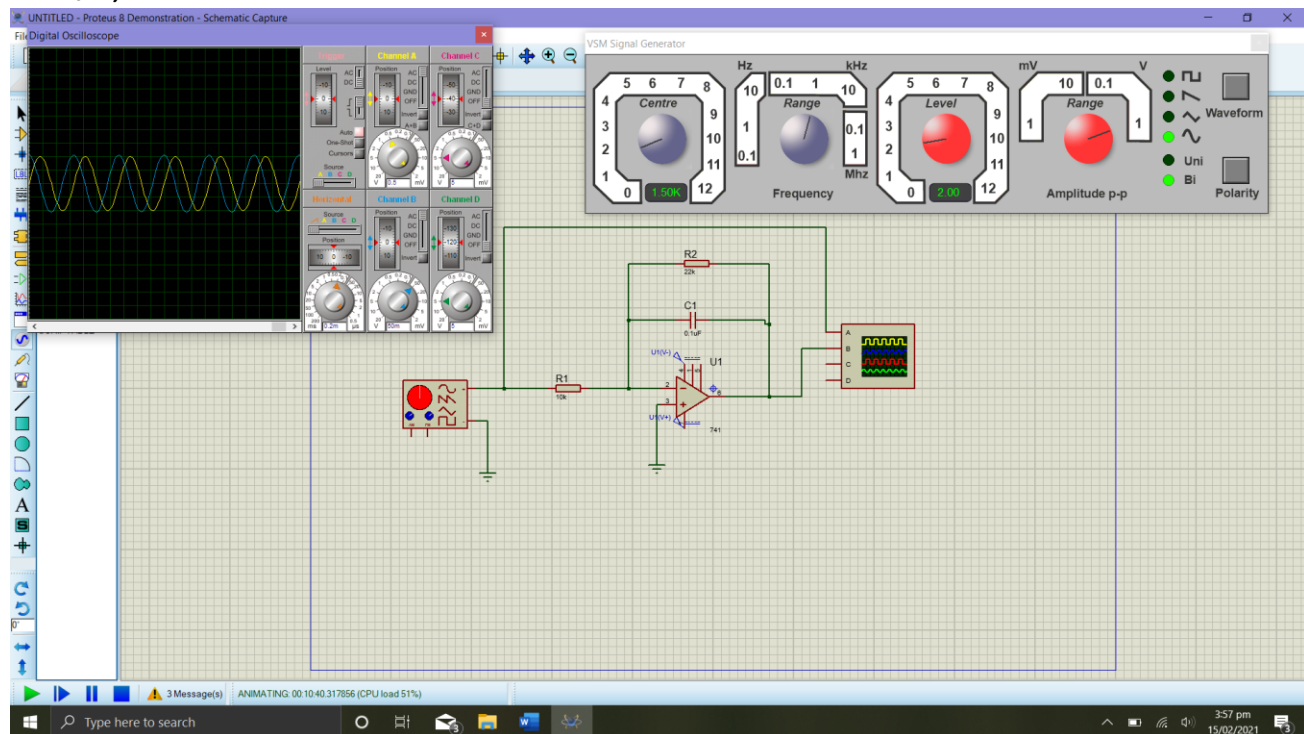

For $V_0=2.5$, $f=2.5\text{kHz}$: -

