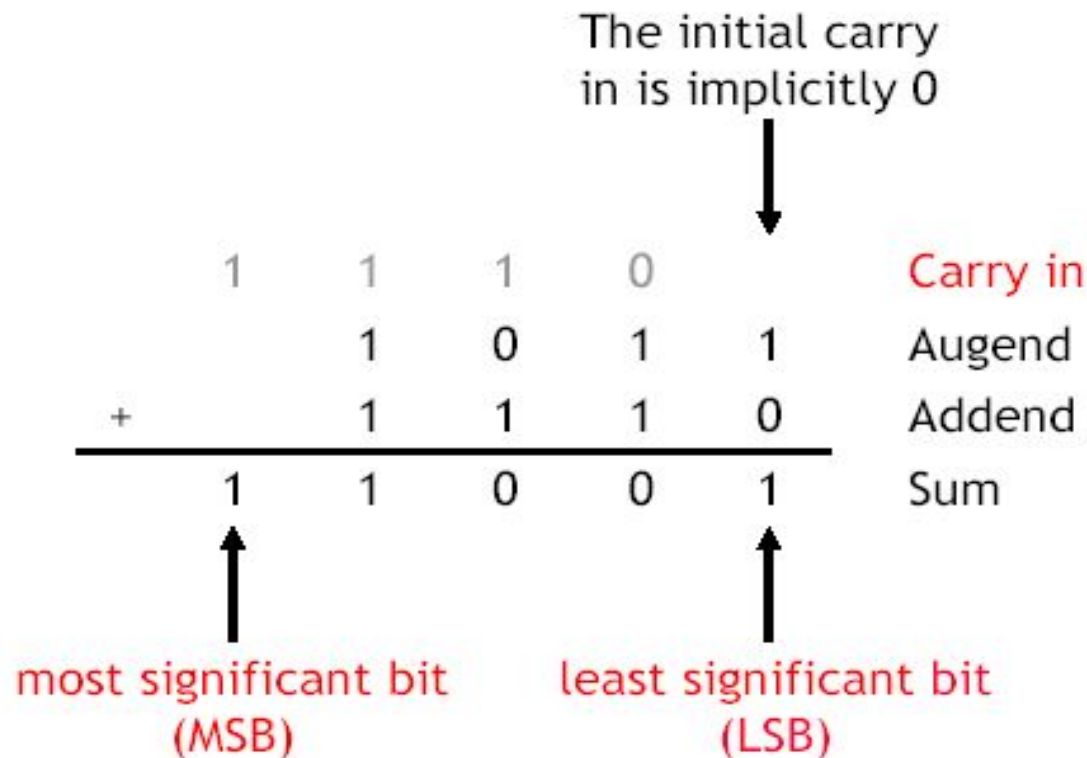


Overview

- Adder
- Ripple Carry Adder
- Subtraction
- Adder/Subtractor

Binary addition by hand

- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example, $1 + 1 = 10$ and you have to carry!



Adder

- Design an Adder for 1-bit numbers?
- **1. Specification:**
 - 2 inputs (X, Y)
 - 2 outputs (C,S)

Adder

- Design an Adder for 1-bit numbers?
- **1. Specification:**
2 inputs (X,Y)
2 outputs (C,S)
- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Adder

- Design an Adder for 1-bit numbers?

- **1. Specification:**


2 inputs (X,Y)

2 outputs (C,S)

- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- **3. Circuit**

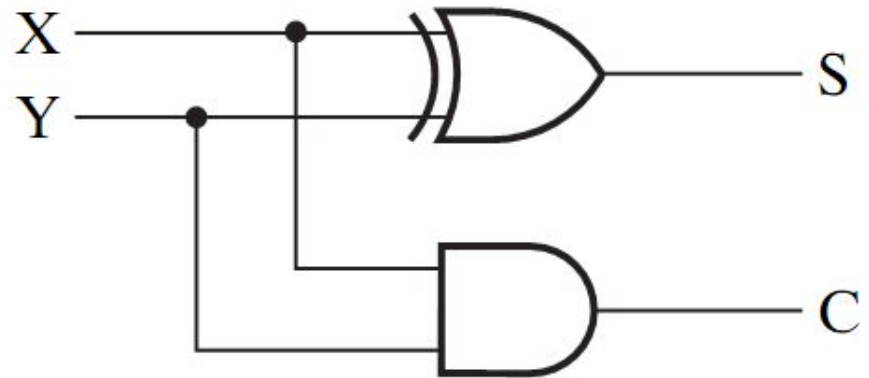

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit
- A truth table and sum of minterm equations for C and S are shown below.

	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10$ →	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11$ →	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= X \oplus Y \oplus Z$$

$$C = X'YZ + XY'Z + XYZ' + XYZ$$

$$= (X'Y + XY') \cdot Z + XY(Z' + Z)$$

$$= (X \oplus Y)Z + XY$$

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$


$$C = (X \oplus Y)Z + XY$$

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = (X \oplus Y)Z + XY$$

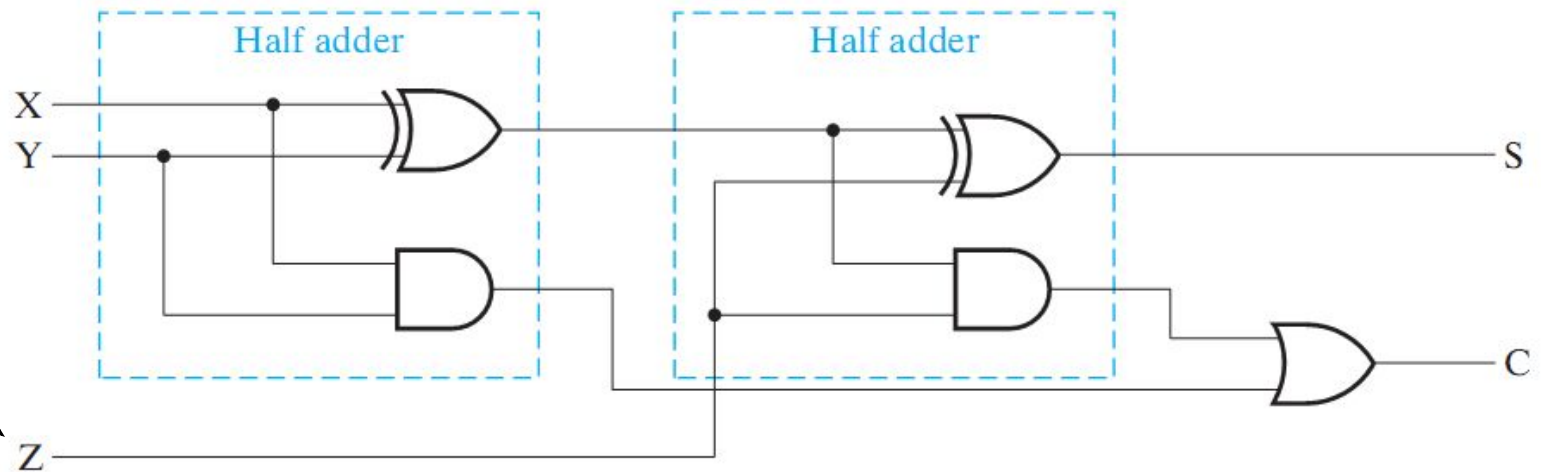

Src: Mano's Book

Bigger Adders

- How to build an adder for n -bit numbers?
 - Example: 4-Bit Adder
 - Inputs ?
 - Outputs ?
 - What is the size of the truth table?
 - How many functions to optimize?

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ? 9 inputs
 - Outputs ? 5 outputs
 - What is the size of the truth table? 512 rows!
 - How many functions to optimize? 5 functions


Ripple Carry Adder

- To add n-bit numbers:
 - Use n Full-Adders
 - The carries propagates as in addition by hand
 - Use Z in the circuit as a C_{in}

- | | | | |
|-------|---|---|---|
| 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| <hr/> | | | |
| 1 | 0 | 1 | 1 |
-
-
-

Ripple Carry Adder

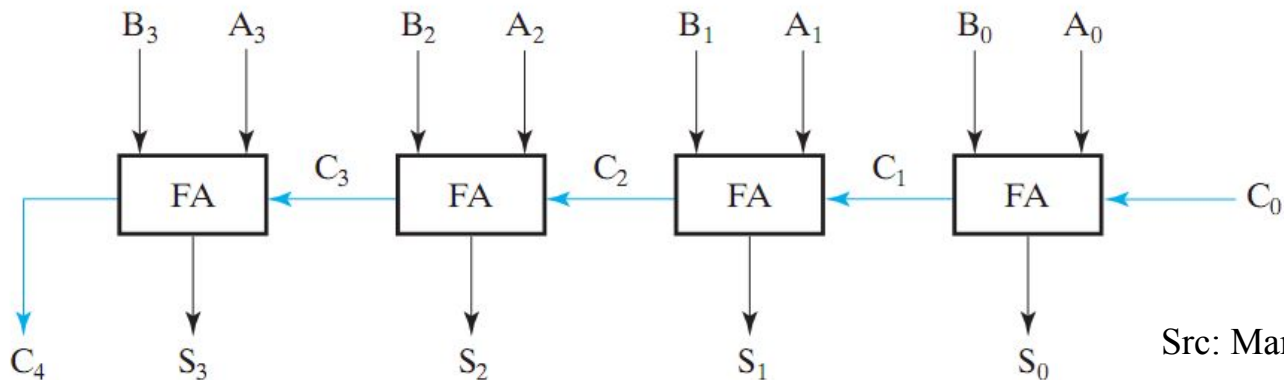- To add n-bit numbers:
 - Use n Full-Adders
 - The carries propagate as in addition by hand



Src: Mano's Book


This adder is called *a 4-bit ripple carry adder*

Subtraction (2's Complement)

- How to build a subtractor using 2's complement?

Subtraction (2's Complement)

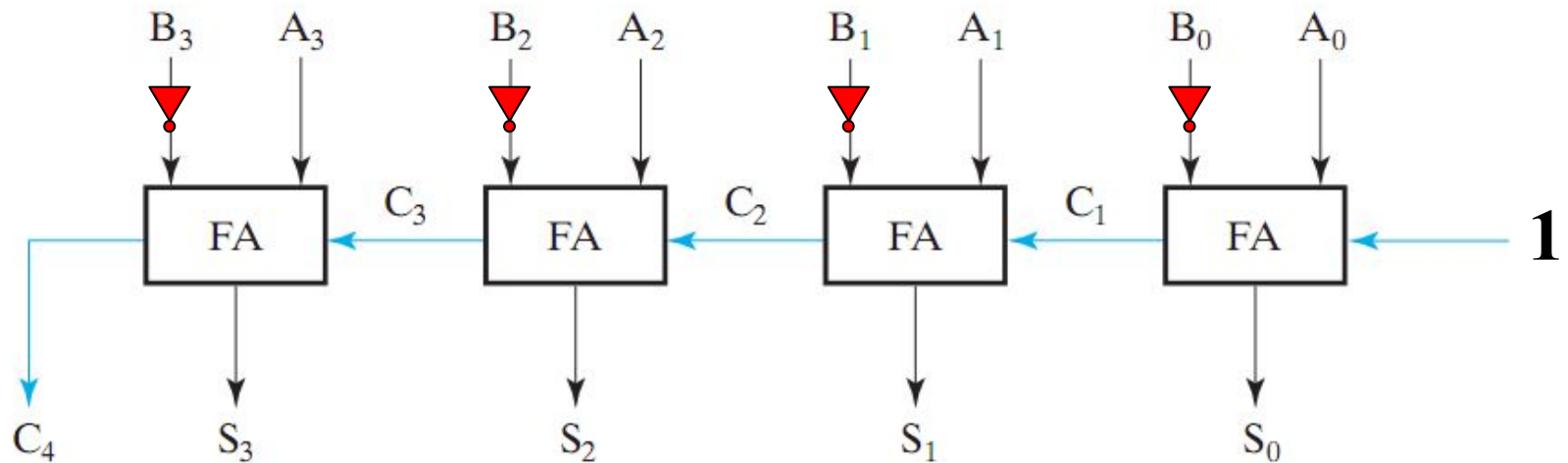- How to build a subtractor using 2's complement?




Src: Mano's Book

$$S = A + (-B)$$

Adder/Subtractor

- How to build a circuit that performs both addition and subtraction?

Adder/Subtractor

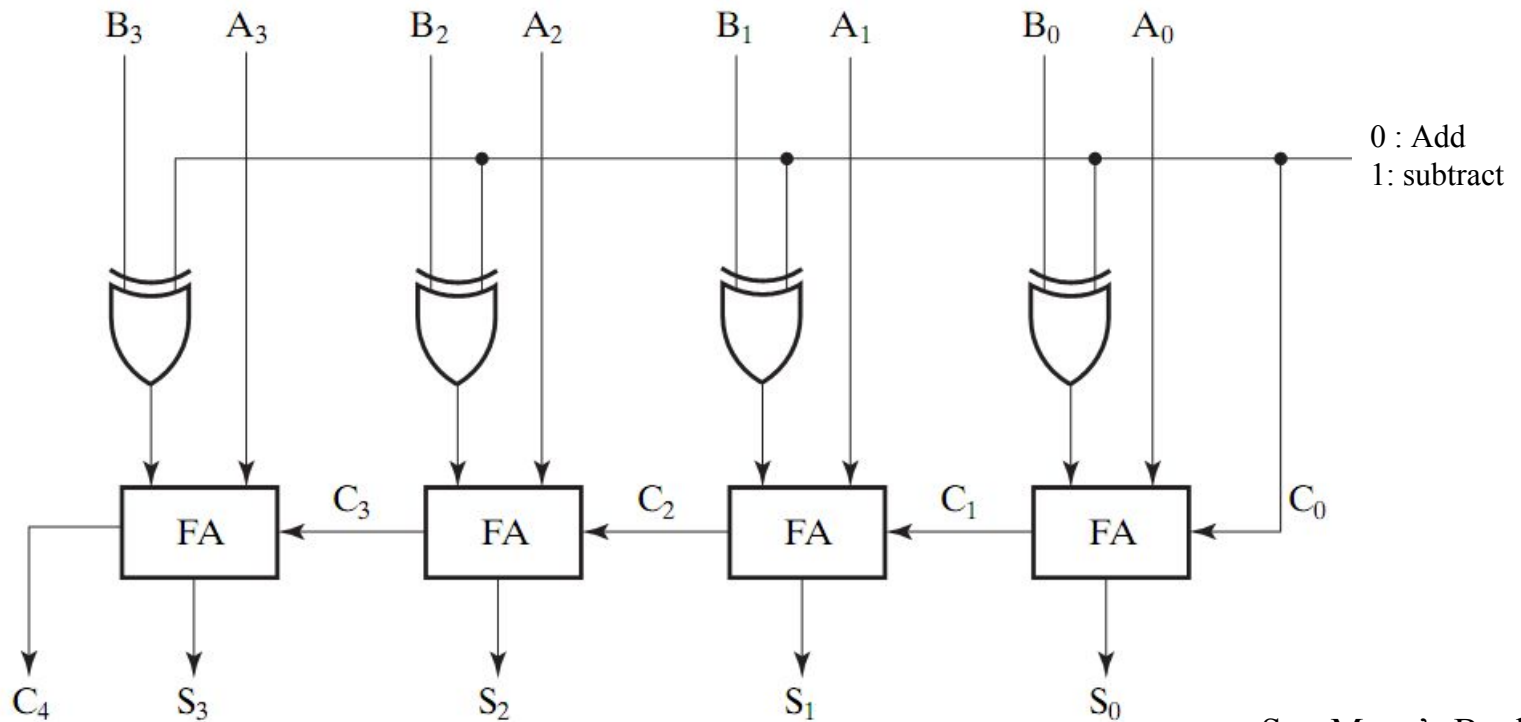

Src: Mano's Book

Using full adders and XOR we can build an Adder/Subtractor!