 


## **LAB REPORT NO 2**



**Spring 2020**

**CSE-202L Digital logic design lab**

Submitted by: **Muhammad Ali**

Registration No:- **19PWCSE1801**

Class Section: A

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

**Engr. Abdullah Hamid**

(December 13, 2020)

Department of Computer Systems Engineering

University of Engineering and Technology, Peshawar

## **LABORATORY EXERCISE # 2**

**TITLE                    “STUDY OF BASIC GATES”**

### **Objectives:**

- To study basic gates.
- To determine the ground and VCC terminal of gates.
- To verify gates with truth table

### **APPARATUS:-**

Power Supply, Breadboard, Connecting Wires.

### **COMPONENTS ICs :-**

7400, 7402, 7404, 7408, 7432, 7486, DIP Switch and LEDs.

### **Theory introduction:-**


Logic gates are the digital circuits with one output and one or more inputs. They are the basic building blocks of any logic circuit. Different logic gates are : AND, OR, NOT, NAND, NOR, EX-OR. Digital circuits have two discrete voltage levels to represent the binary digits (bits) 1 and 0. All digital circuits are switching circuits. Instead of mechanical switches, they use high-speed transistors to represent either an ON condition or an OFF condition. Various types of logic, representing different technologies, are available to logic designers. The choice of a particular family is determined by factors such as speed, cost, availability, noise immunity, and so forth. The key requirement within each family is compatibility; that is, there must be consistency within the logic levels and power supplies of various integrated circuits made by different manufacturers. The experiments in this lab use primarily transistor-transistor logic, or TTL. The detailed performance characteristics of TTL depend on the particular subfamily. However, all TTL is designed to operate from a 5 V power supply, and the logic levels are the same for all TTL integrated circuits.

## Verification of OR gate with truth table:-

### OR gate:-

Logic eqn.  $Y=A+B$ . The output of OR gate is true when one of the inputs A and B or both the inputs are true.  $Y=1$  if  $A=1$  Or  $B=1$  Or both  $A=1$   $B=1$ .

### IC PINOUTS

 

### TRUTH/FUNCTION

Table

A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1




Note:- input =10

### Procedure:-

- First we insert OR gate in the middle rows at breadboard.
- The 14<sup>th</sup> terminal (VCC) of gate is connected with positive terminal of the power supply and the 7<sup>th</sup> (ground) is connect with negative of power supply.
- We give two input to terminals 1<sup>st</sup> and 2<sup>nd</sup>, and take output from 3<sup>rd</sup> terminal by inserting LED.
- Input of 0 means ground and input of 1 means VCC.
- We have four possible combine input of two inputs, i-e (00,01,10,11) and output by LED with (OFF,ON,ON,ON) respectively.
- This is how we verify OR gate with truth table.
- Same steps are repeated for verification of AND,NOT,NOR,NAND,XOR etc.
 
### AND gate:-


Function expression for AND gate is  $y=A.B$ , the output of and gate is  $Y=0$  if A Or B is equal to 0, and  $Y=1$  when both  $A=1$  and  $B=1$



A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1
 
### NOT:-


Logic eqn.  $Y = A'$ . The output of NOT gate is complement of the input.



A	B	$Y=A'$
0	1	0
1	1	0
 
### NOR:-


Logical eqn.  $Y = \overline{A+B}$ . The output of NOR gate is true ( $Y=1$ ) when both the inputs are low. otherwise  $Y=0$ .



A	B	$Y=(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0
 
### NAND:-


Logic equation.  $Y = \overline{A \cdot B}$ . The output of NAND gate is true when one of the inputs or both the inputs are low.



A	B	$Y = (A \cdot B)'$
0	0	1
0	1	1
1	0	1
1	1	0
 
### EX-OR:-

Logic eqn.  $Y = \overline{A}B + A\overline{B}$ . The output of EX-OR gate is true when both the inputs are dissimilar.



A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

### Conclusion:-

After performing the experiment for OR gate and then repeating all experimental steps for other gates (AND, NAND, NOR, EX-OR, NOT) we prove all the truth table for each gate separately.



## REVIEW QUESTIONS:-

- 1) A burglar alarm for a car has a normally LOW (grounded) switch on each of four doors. If any door is opened, the output of that switch goes HIGH. The alarm is set off with an active LOW output. What type of gate will provide this logic?

Answer:-


OR gate will provide this logic of a burglar alarm for a car. Because switch of the alarm has to become high when any door is opened, if any door is open the switch will output high.

- 2) If more than two input AND & OR gates are available, how will you connect its inputs so that they work as two input gates? Perform it for three and four input AND & OR gates.

Answer:-

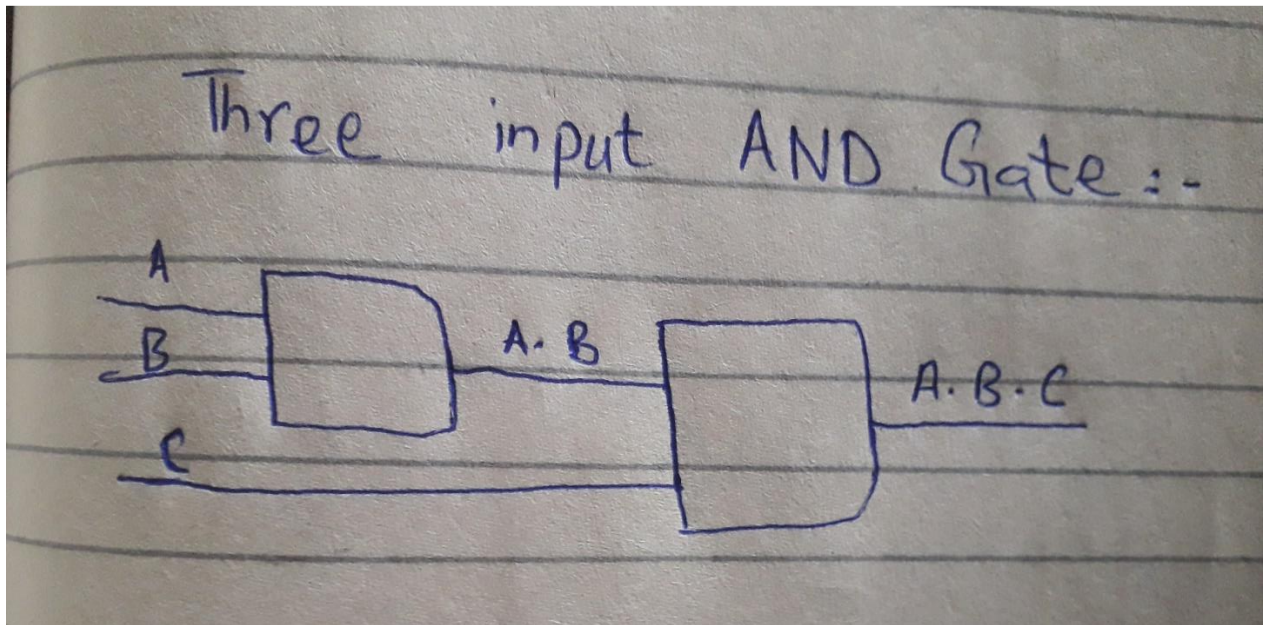**For three AND gate:-**

We can connect three input using two AND gates which work as two inputs. A.B is the first input and C is the second input. As shown in the diagram.



### For four input OR gate:-

By using three OR gates we can connect four inputs gate to two input gate, first input is  $A+B+C$  and the second input is  $D$ . As shown in the written diagram.

