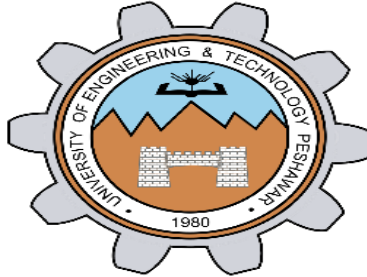


Lab report no 11



Fall 2021

Computer Architecture and organization Lab

Submitted By

Names	Registration No
Muhammad Ali	19pwcse1801

Section: A

Date:23,2,21

Submitted to: Dr Amaad khalil

Department of Computer Systems Engineering

University of Engineering and Technology, Peshawar

Task no 1 (2x1): -

Code: -

Mux2x1 module: -

```
module mux2x1(A,B,set,f);  
input A,B,set;  
output f;  
wire nset,f1,f2;  
not n1(nset,set);  
and a1(f1,A,nset);  
and a2(f2,B,set);  
or o1(f,f1,f2);  
endmodule
```

Stim module: -


```
module stim();  
reg A,B,set;  
wire f;  
mux2x1 t(A,B,set,f);  
initial  
begin  
$display ("A B set f");  
  
A=0;B=0; set=0;  
#10 $display("%b %b %b %b",A,B,set,f);
```

```

A=0;B=0; set=1;
#10 $display("%b %b %b %b",A,B,set,f);
A=0;B=1; set=0;
#10 $display("%b %b %b %b",A,B,set,f);
A=0;B=1; set=1;
#10 $display("%b %b %b %b",A,B,set,f);
A=1;B=0; set=0;
#10 $display("%b %b %b %b",A,B,set,f);
A=0;B=1; set=1;
#10 $display("%b %b %b %b",A,B,set,f);
A=0;B=0; set=1;
#10 $display("%b %b %b %b",A,B,set,f);
A=1;B=1; set=1;
#10 $display("%b %b %b %b",A,B,set,f);
end
endmodule

```

Design circuit: -

 

Task no 1 (4x1): -

Code: -

Mux4x1 module: -

```
module mux4x1(A,B,C,D,set0,set1,f);  
input A,B,C,D,set0,set1;  
output f;  
wire nset0,nset1,f1,f2,f3,f4;  
not n1(nset0,nset1,set0,set1);  
and a1(f1,nset1,A,nset0);  
and a2(f2,nset1,B,set0);  
and a3(f3,set1,C,nset0);  
and a4(f4,set1,D,set0);  
or o1(f,f1,f2,f3,f4);  
endmodule
```

Stim module: -


```
module stim();  
reg A,B,C,D,set0,set1;  
wire f;  
  
mux4x1 t(A,B,C,D,set0,set1,f);  
  
initial  
begin  
$display ("A B C D set0 set1 f");  
  
A=0; B=0; C=0; D=0;set0=0; set1=0;  
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);  
A=0;B=0; C=0; D=0; set0=0; set1=1;  
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
```

```

A=0;B=0; C=0; D=1; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=0;B=0; C=1; D=0; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=0;B=1; C=0; D=0; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=1;B=0; C=0; D=0; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=0;B=0; C=1; D=1; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=0;B=1; C=0; D=1; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=0;B=0; C=1; D=0; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=0;B=1; C=1; D=0; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=1;B=0; C=0; D=1; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=1;B=1; C=0; D=1; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=1;B=1; C=1; D=0; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
A=1;B=1; C=1; D=1; set0=0; set1=1;
#10 $display("%b %b %b %b %b %b %b",A,B,C,D,set0,set1,f);
end
endmodule

```

Design circuit: -

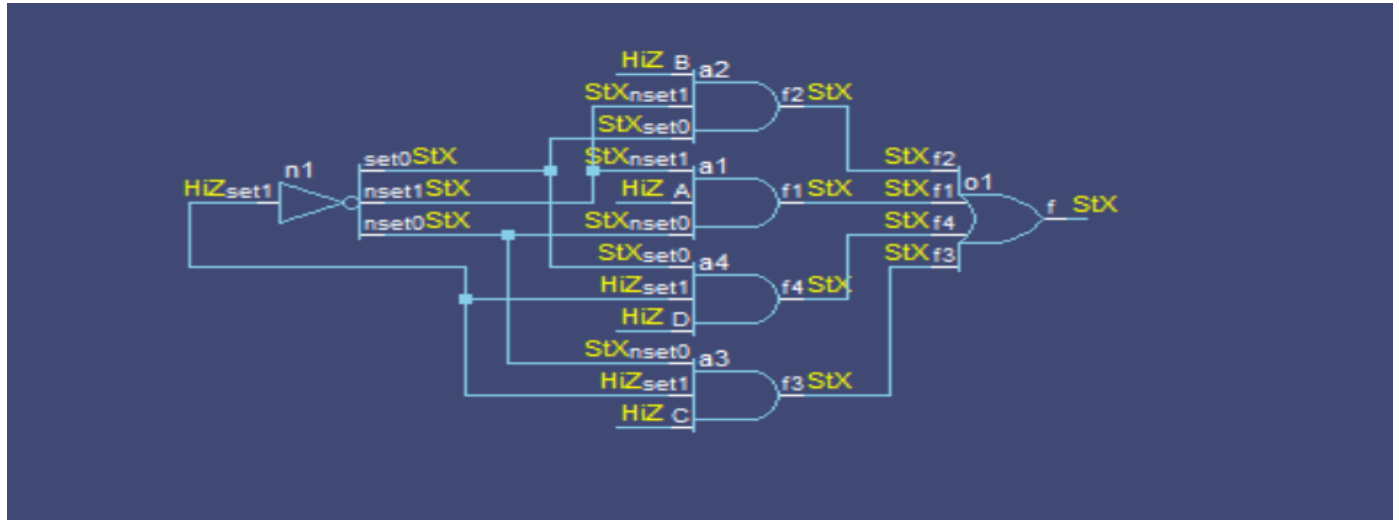

Task no 2 (Half adder): -

Code: -

Half adder module: -

```
module halfadder(A,B,f1,f2);
```

```
input A,B;
```

```
output f1,f2;
```

```
and a1(f1,A,B);
```

```
xor a2(f2,A,B);
```

```
endmodule
```

Stim module: -

```
module stim();
```

```
reg A,B;
```

```
wire f1,f2;
```

```
halfadder t(A,B,f1,f2);
```

```
initial
```

```
begin
```

```
$display ("A B f1 f2");
```

```
A=0;B=0;
```

```
#10 $display("%b %b %b %b",A,B,f1,f2);
```

```
A=0;B=1;
```

```
#10 $display("%b %b %b %b",A,B,f1,f2);
```

```
A=1;B=0;
```

```
#10 $display("%b %b %b %b",A,B,f1,f2);
```

```
A=1;B=1;
```

```
#10 $display("%b %b %b %b",A,B,f1,f2);
```

```
end
```

```
endmodule
```

Design circuit: -



Task no 2 (Half subtractor): -

Code: -

Half subtractor module: -

```
module halfsub(A,B,S,C);
```

```
input A,B;
```

```
output S,C;
```

```
not noot(nB,B);
```

```
xor subtracte(S,A,B);
```

```
and carry(C,A,nB);
```

```
endmodule
```

Stim module: -

```
module stimhalfsub();
```

```
reg A,B;
```

```
wire S,C;
```

```
halfsub halfsubtractor(A,B,S,C);
```

```
initial
```

```
begin
```

```
$display ("A B Subtract Carry");
```

```
A=0;B=0;
```

```
#10 $display("%b %b %b %b",A,B,S,C);
```


A=0;B=1;

#10 \$display("%b %b %b %b",A,B,S,C);

A=1;B=0;

#10 \$display("%b %b %b %b",A,B,S,C);

A=1;B=1;

#10 \$display("%b %b %b %b",A,B,S,C);

end

endmodule

Design circuit: -

