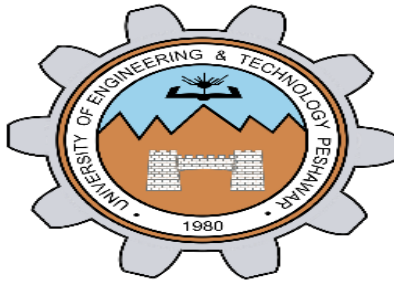


LAB REPORT NO 11



Spring 2020

CS-II lab

Submitted by: **Muhammad Ali**

Registration No: **19PWCSE1801**

Class Section: A

Submitted to:

Engr. Faiz ullah

(07/03/ 2021)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Lab 11

High Pass Filter

It is a frequency selective circuit, which passes signals of frequencies above its low cut off frequency (f_L) and attenuates signals of frequencies below f_L .

Objectives:

To study the Active High pass filter and to evaluate:

- Low cutoff frequency of High pass filter.
- Pass band gain of High pass filter.
- Plot the frequency response of High pass filter.

Equipment:

1. DC power supplies +15V, -15V from external source
2. Function generator
3. Oscilloscope
4. Digital Multimeter

Components:

1. Resistance 10k Ω
2. Resistance 22k Ω
3. Capacitor 0.01 μ F
4. LM 741

Equation of High pass filter

$$\frac{V_{out}}{V_{in}} = \frac{A_F}{1+j(f/f_L)} \quad 1$$

$$\frac{V_{out}}{V_{in}} = \frac{A_F}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}} \quad 2$$

V_{in} = Input signal Voltage

V_{out} = Output signal Voltage

$|V_{out}/V_{in}|$ = Gain of filter as a function of frequency

$A_F = 1 + R_F/R_1$ = pass band gain of filter

f = frequency of input signal


$f_L = 1/2\pi RC$ = Low cut off frequency, 3-dB frequency, corner frequency

Operation of high pass filter using equation 2.1.

At low frequencies $f < f_L$: $|V_{out}/V_{in}| < A_F$

2. At $f = f_L$ $|V_{out}/V_{in}| = 0.707 * A_F$ (Approx.)

3. At $f > f_L$ $|V_{out}/V_{in}| = A_F$

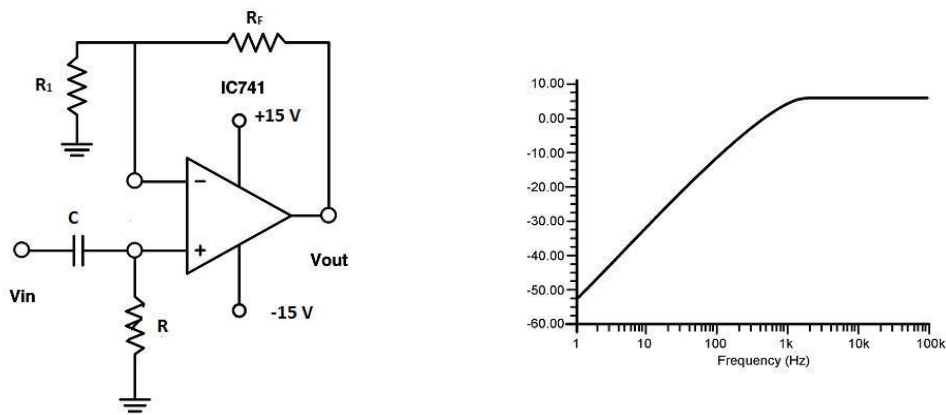

In ideal high pass filter, when $f < f_L$ gain is increased at a constant rate with an increase in frequency. At f_L the gain is $0.707 * A_F$, and above f_L it has constant gain of A_F . Below f_L when input frequency is increased tenfold (one decade), the voltage gain is multiplied by 10.

Gain (dB) = $20 \log |V_{out} / V_{in}|$

i.e. Gain Roll off rate is $-20\text{dB} / \text{decade}$.

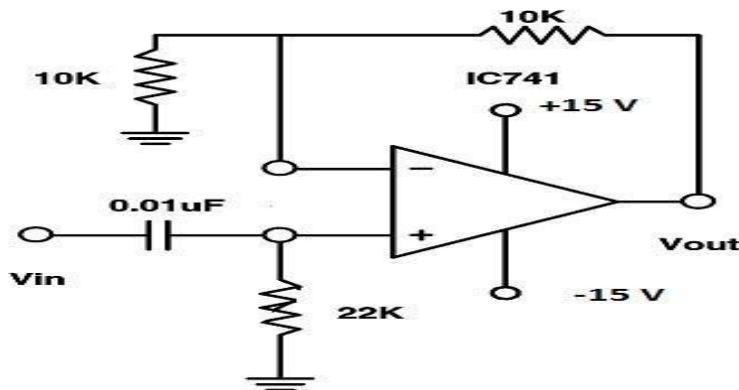


Figure 2

Procedure:

1. Connect the circuit as shown in Figure 2.
2. Switch ON the power supply.
3. Connect a sinusoidal signal of amplitude 1V (p-p) of frequency 1KHz to V_{in} of High pass filter from function generator.
4. Connect Ch-1 of oscilloscope to the signal source.
5. Observe output on Ch-2 of oscilloscope.
6. Increase the frequency of input signal step by step and observe the effect on output V_{out} on oscilloscope.
7. Tabulate values of V_{out} , gain, gain (dB) at different values of input frequency shown in observation Table 2.
8. Plot the frequency response of High pass filter using the data obtained at different input frequencies.

Theoretical Calculations:

Calculate all the following values

1. Pass band gain of High pass filter $A_F = 1 + R_F / R_1$
2. Pass band gain (dB) $= 20 \log |V_{out} / V_{in}|$
3. Low cutoff frequency $f_L = 1/2\pi RC$
4. Gain at Low cutoff frequency $f_L = 0.707 * A_F$
5. Roll off rate $= -20\text{db/decade}$

Results:

	Theoretical	Practical
Pass band gain(A_t)	2	2.09
Pass band gain (A_t) in db	6.02	6.02
Low cutoff frequency(f_L)	723.7	719.5
Gain at 3db frequency f_H in db	3	2.922

For $V_{in} = 1\text{v}$ (peak to peak): -

Sr. No.	Input Frequency (Hz)	V_{out}	$ V_{out}/V_{in} = \text{Gain}$	$\text{Gain (dB)} = 20 \log V_{out} / V_{in} $
1	300	1	1	0
2	500	1.2	1.2	1.5
3	700	1.5	1.5	3.52
4	1k	1.9	1.9	5.575
5	5k	2.09	2.09	6.40
6	10k	2.00	2.00	6.02
7	15k	2.00	2.00	6.02

Table 2

