

## ***Lab 3***

# **De-Morgan's Theorem**

### **OBJECTIVE**

After completing this experiment, you will be able to:

- Experimentally verify the De-Morgan's theorems using two input variables

### **COMPONENTS REQUIRED**

- 7432 quad 2-input OR gate
- 7404 hex inverter
- LED
- 7430 quad 2-input AND gate
- DIP switch
- Three 1 kΩ resistors

### **DE-MORGAN'S THEOREM**

- $(X + Y)' = X' \cdot Y'$  ..... (a)
- $(X \cdot Y)' = X' + Y'$  ..... (b)

### **PROCEDURE**

- Build the circuit for left part of equation (a) as shown in figure 3.1 and monitor the behavior of LED for different test inputs
- Then complete the circuit of figure 3.2 for the right part of equation (a) and complete the truth table 3.1 by testing each combination of inputs of appropriate switches
- Compare both the column results and check whether equation (a) is verified or not
- Repeat the above process by building the circuits of figure 3.3 and 3.4 and comparing its results for De-Morgan's theorem verification of equation (b) .

## LOGIC CIRCUIT DIAGRAMS

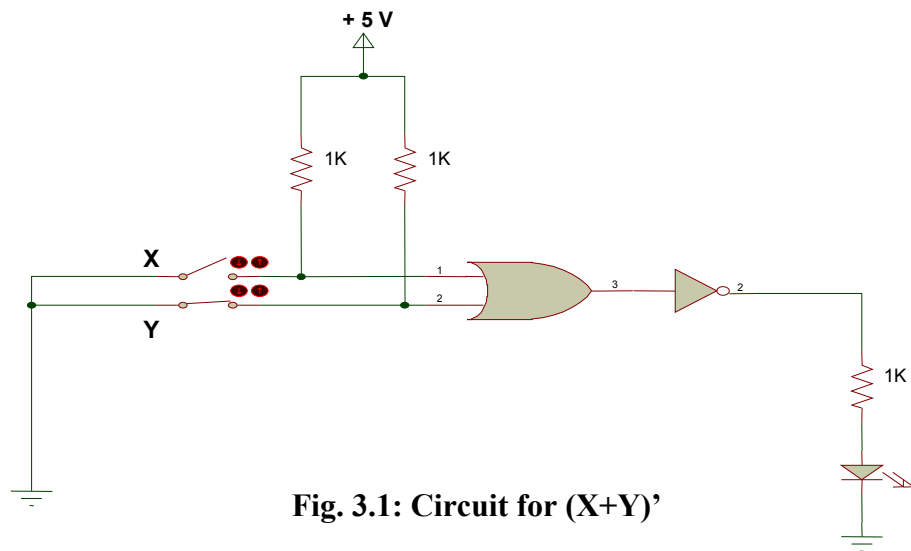


Fig. 3.1: Circuit for  $(X+Y)'$


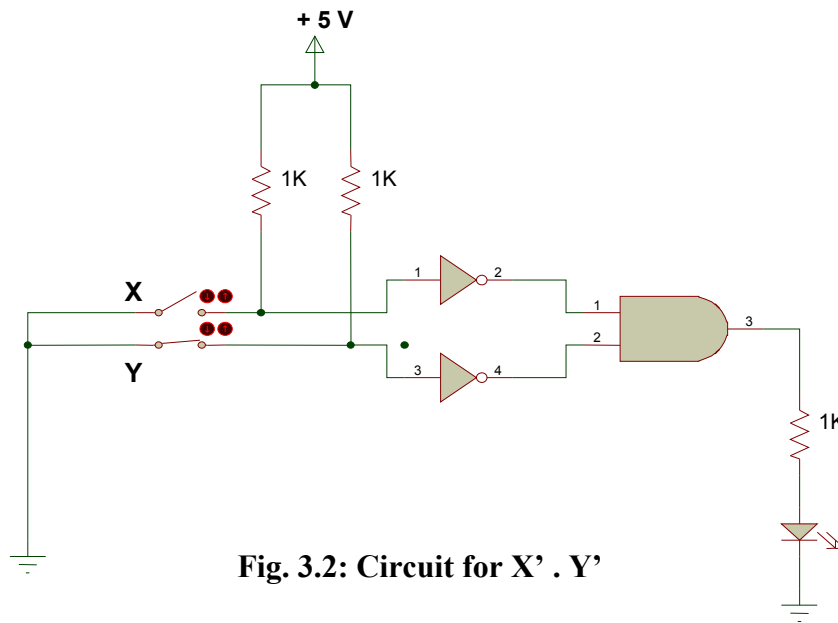



Fig. 3.2: Circuit for  $X' \cdot Y'$

Truth Table 3.1

X	Y	$(X + Y)'$	$(X' \cdot Y')$
0	0		
0	1		
1	0		
1	1		

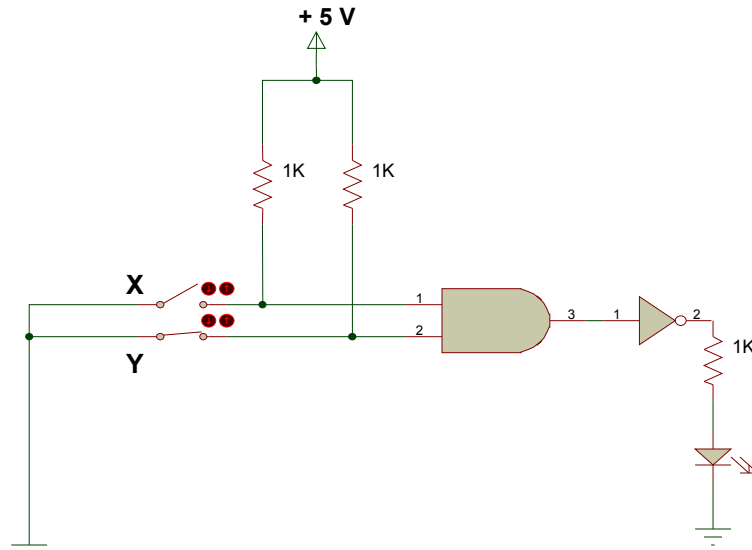

**Fig. 3.3: Circuit for  $(X.Y)'$**

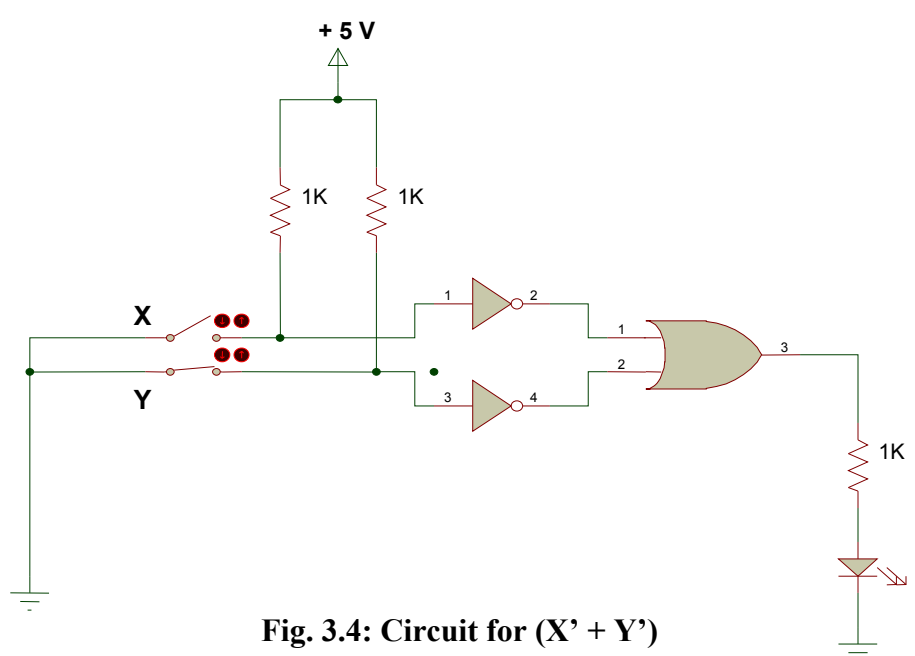

**Fig. 3.4: Circuit for  $(X' + Y')$**

**Truth Table 3.2**

X	Y	$(X . Y)'$	$(X' + Y')$
0	0		
0	1		
1	0		
1	1		

## REVIEW QUESTIONS

- Simplify the expression using De-Morgan's theorems and verify the two expressions experimentally.

$$F = ((A \cdot B)' + A)'$$

- Determine experimentally whether the given circuits are equivalent. Then use De-Morgan's theorem to prove your answer algebraically.

