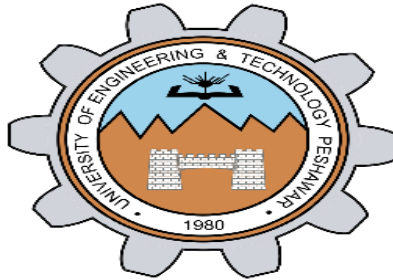


LAB REPORT NO 2



Spring 2020

CSE-202L Digital logic design lab

Submitted by: **Muhammad Ali**

Registration No:- **19PWCSE1801**

Class Section: A

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

Engr. Abdullah Hamid

(December 19, 2020)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Lab 3

De-Morgan's Theorem

OBJECTIVE

After completing this experiment, you will be able to:

- Experimentally verify the De-Morgan's theorems using two input variables

COMPONENTS REQUIRED

- 7432 quad 2-input OR gate
- 7404 hex inverter
- LED
- 7430 quad 2-input AND gate
- DIP switch
- Three 1 k Ω resistors

DE-MORGAN'S THEOREM

- $(X + Y)' = X' \cdot Y'$ (a)
- $(X \cdot Y)' = X' + Y'$ (b)


PROCEDURE

- Build the circuit for left part of equation (a) as shown in figure 3.1 and monitor the behavior of LED for different test inputs
- Then complete the circuit of figure 3.2 for the right part of equation (a) and complete the truth table 3.1 by testing each combination of inputs of appropriate switches
- Compare both the column results and check whether equation (a) is verified or not
- Repeat the above process by building the circuits of figure 3.3 and 3.4 and comparing its results for De-Morgan's theorem verification of equation (b) .

DE-MORGAN'S THEOREM


$(X+Y)' = X' \cdot Y'$ eq. A

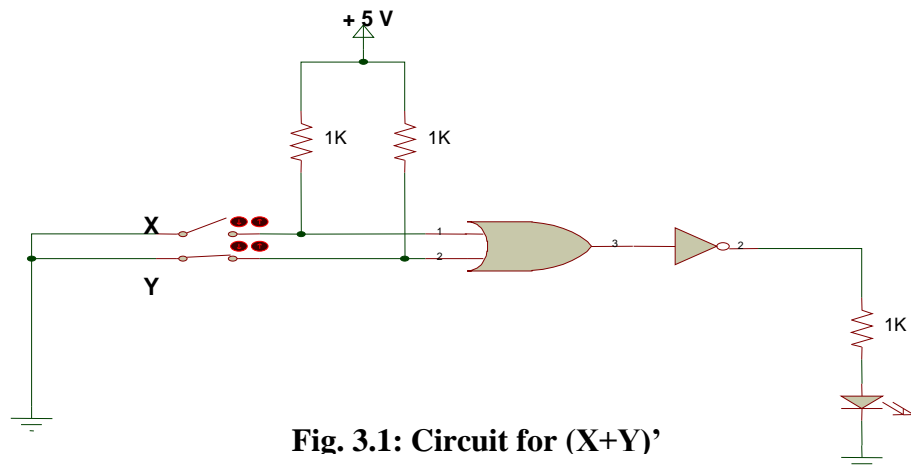For left hand side of equation (A):-
logic circuit diagrams:-



+ 5 V

Experimental circuit:-

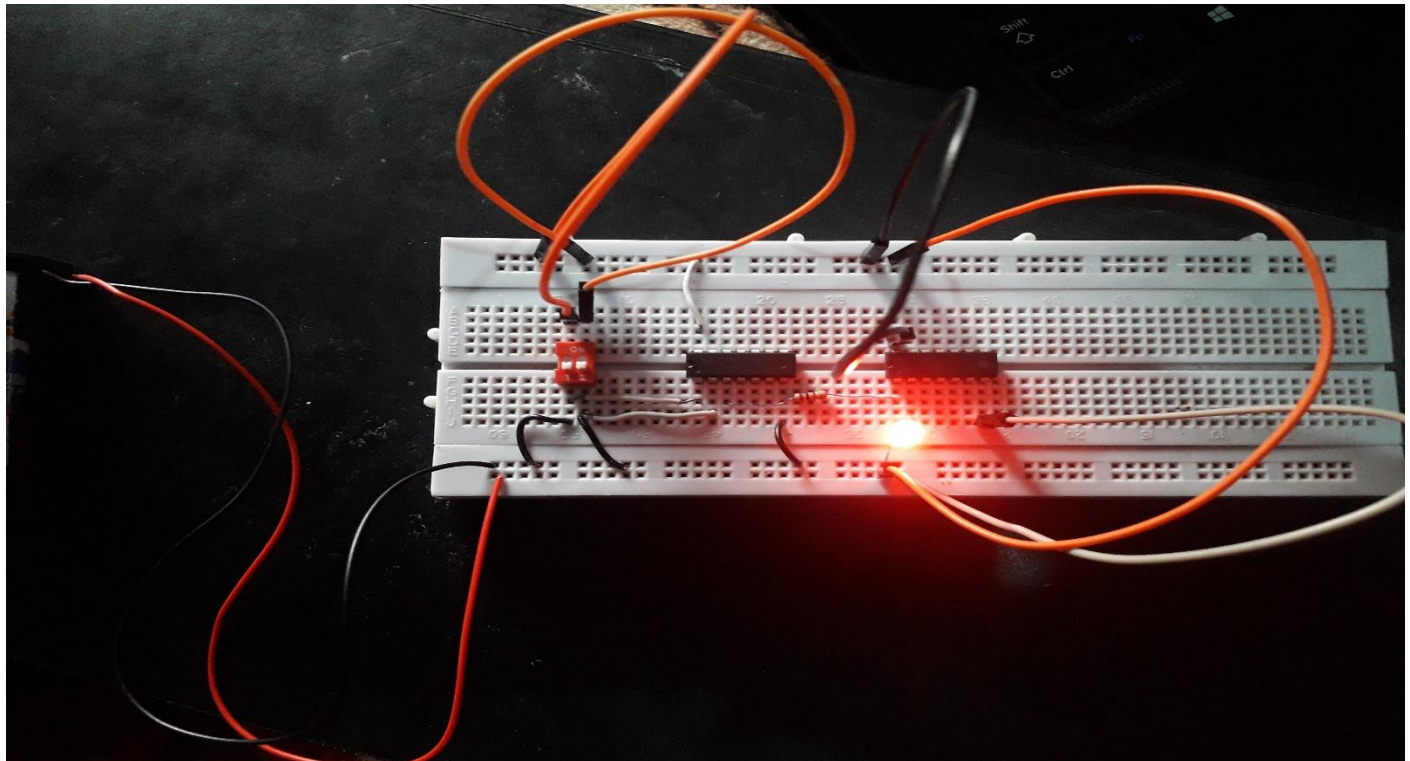

For right hand side of equation (A):-
logic circuit diagrams:-


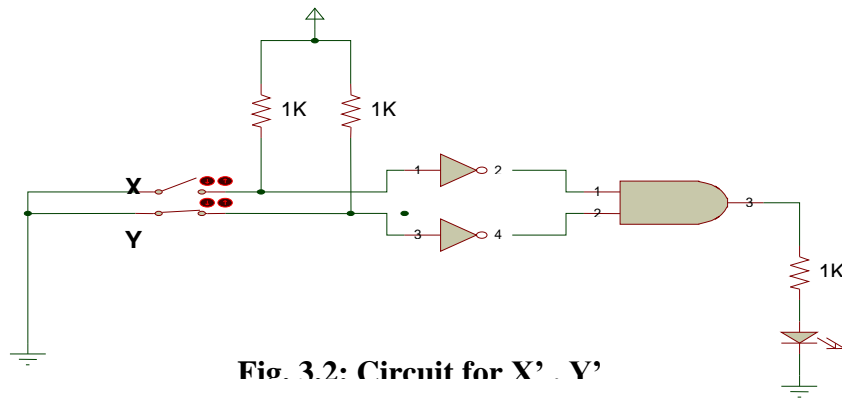


Fig. 3.2: Circuit for $X' \cdot Y'$

Experimental circuit:-

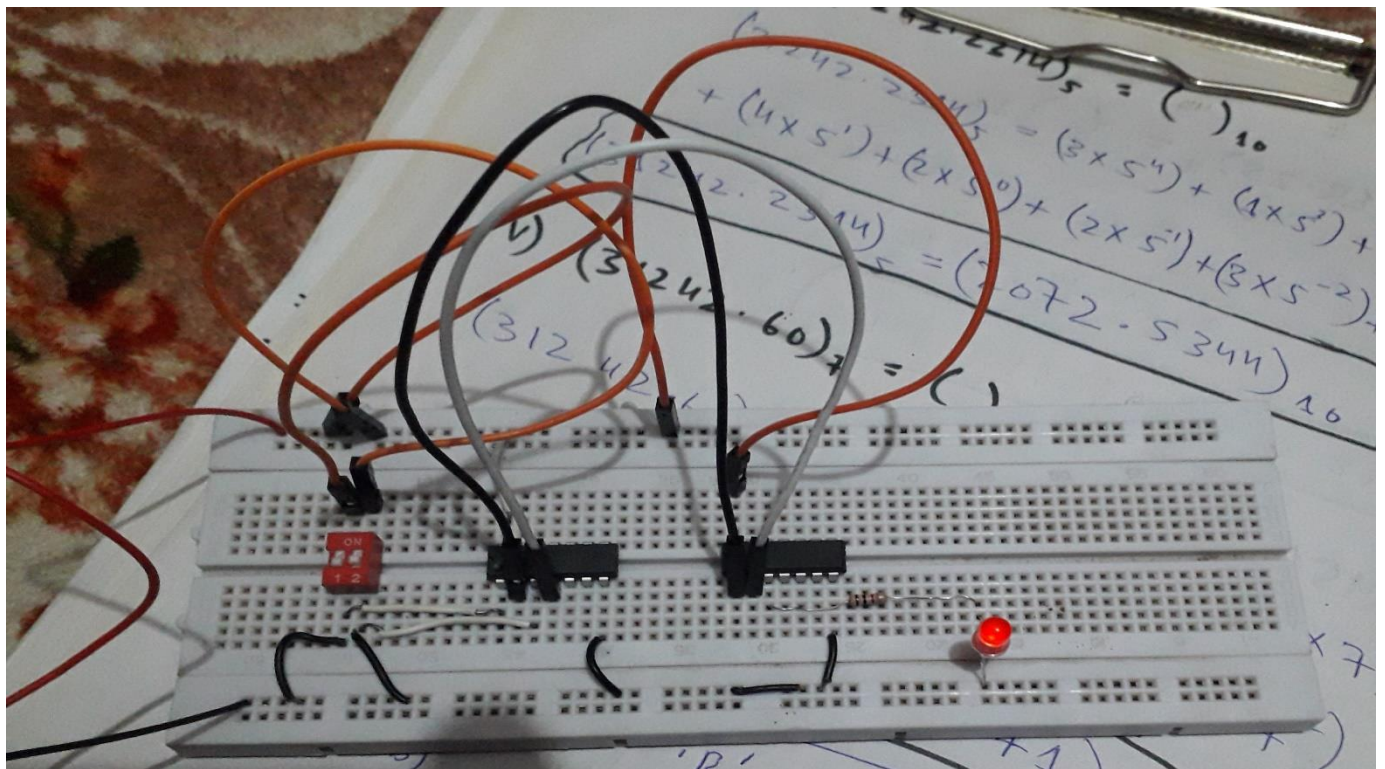

Experimental verified truth table:-


X	Y	$(X + Y)'$	$(X' \cdot Y')$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

2


DE-MORGAN'S THEOREM:-

$(X \cdot Y)' = X' + Y'$ eq. B

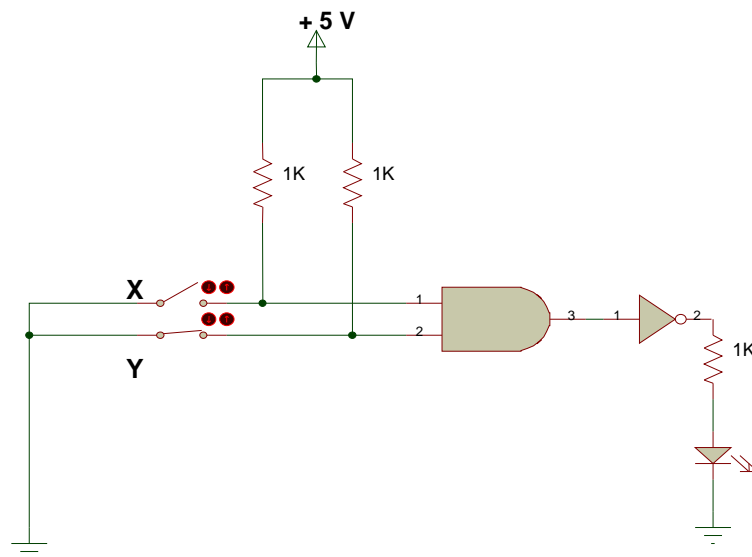For left hand side of equation (B):-
logic circuit diagrams:-



Experimental circuit:-

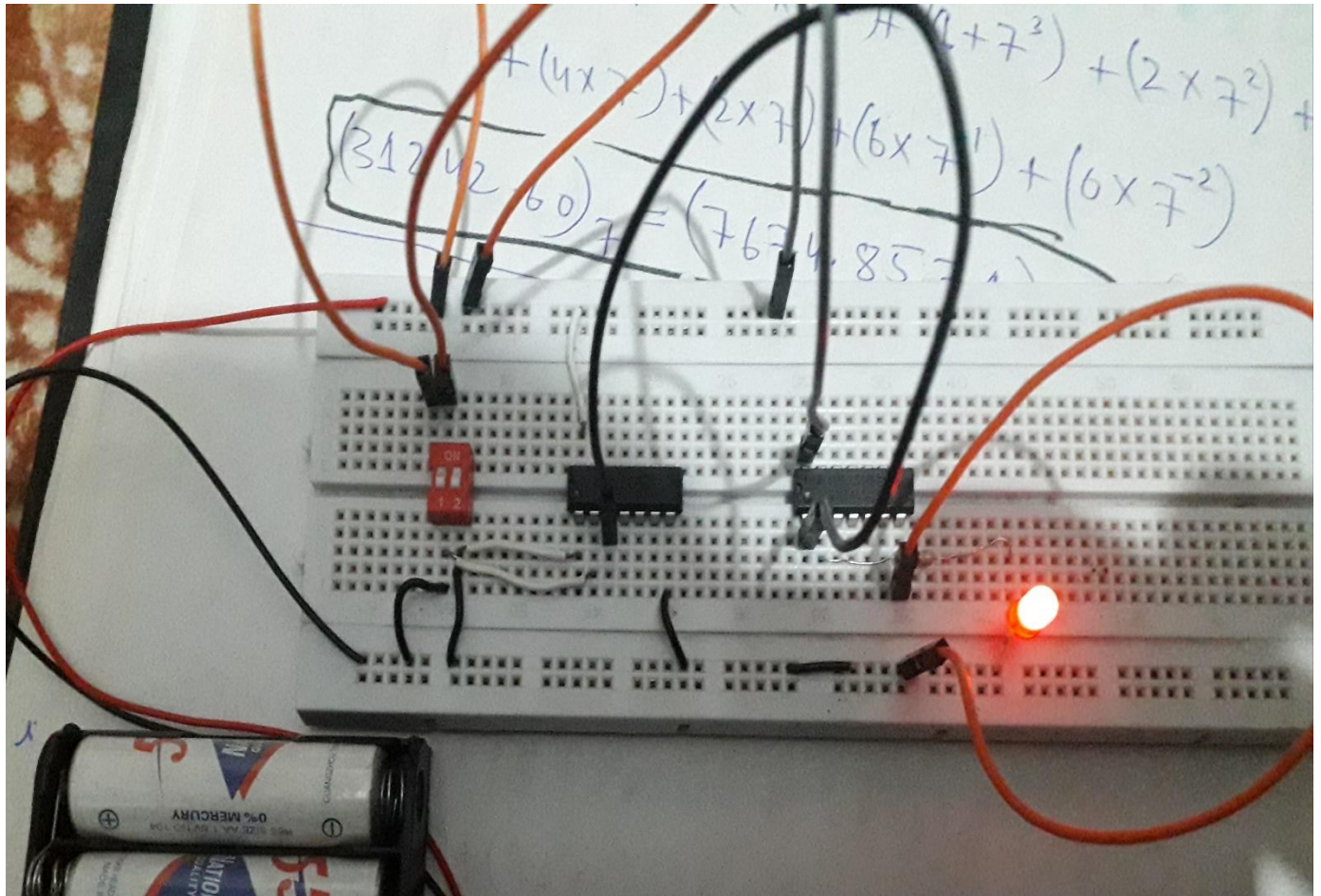

For right hand side of equation (B):-
logic circuit diagrams:-

Fig. 3.3: Circuit for $(X.Y)'$


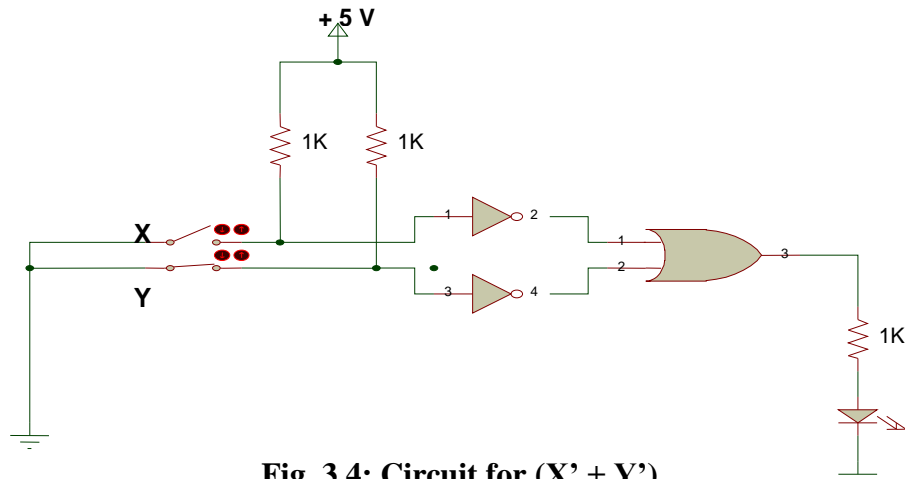


Fig. 3.4: Circuit for $(X' + Y')$

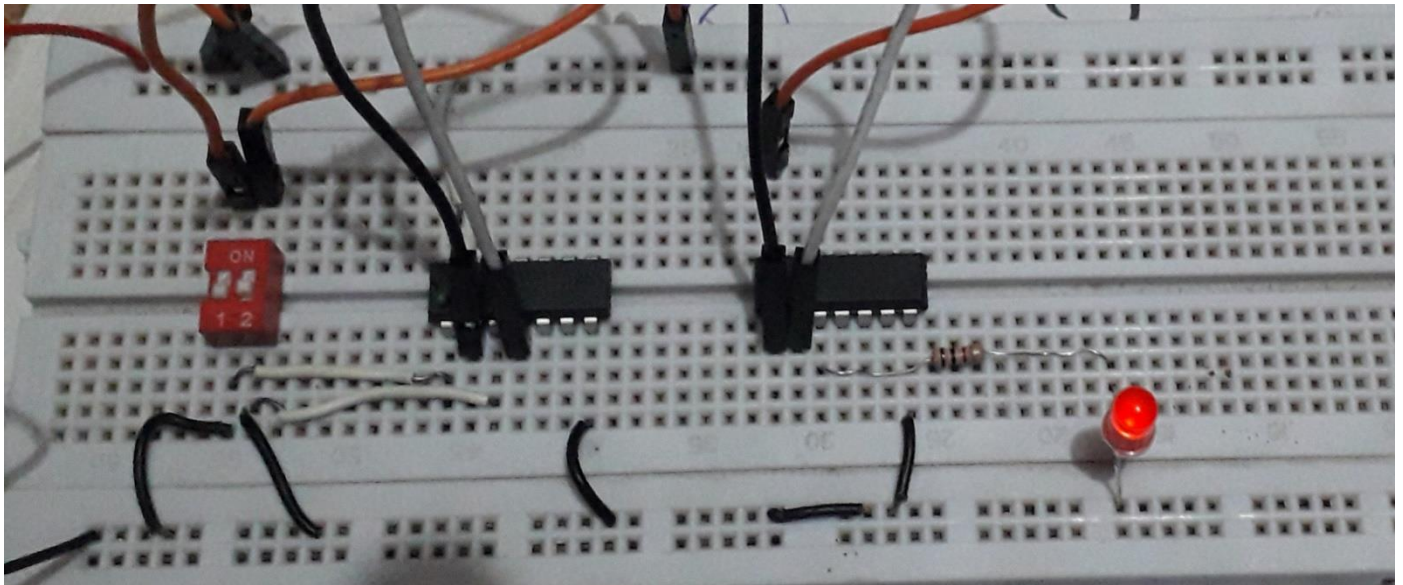

Experimental circuit:-

X	Y	(X . Y)'	(X' + Y')
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

3

REVIEW QUESTIONS

- Simplify the expression using De-Morgan's theorems and verify the two expressions experimentally.

$$F = ((A \cdot B)' + A)'$$

Simplification:-

$$F = ((A \cdot B)' + A)'$$

$$= ((A \cdot B)')' \cdot A'$$


$$= A \cdot B \cdot A'$$

$$= 0 \cdot A$$

$$= 0$$


$$(A \cdot A' = 0)$$

Experimental circuit:-

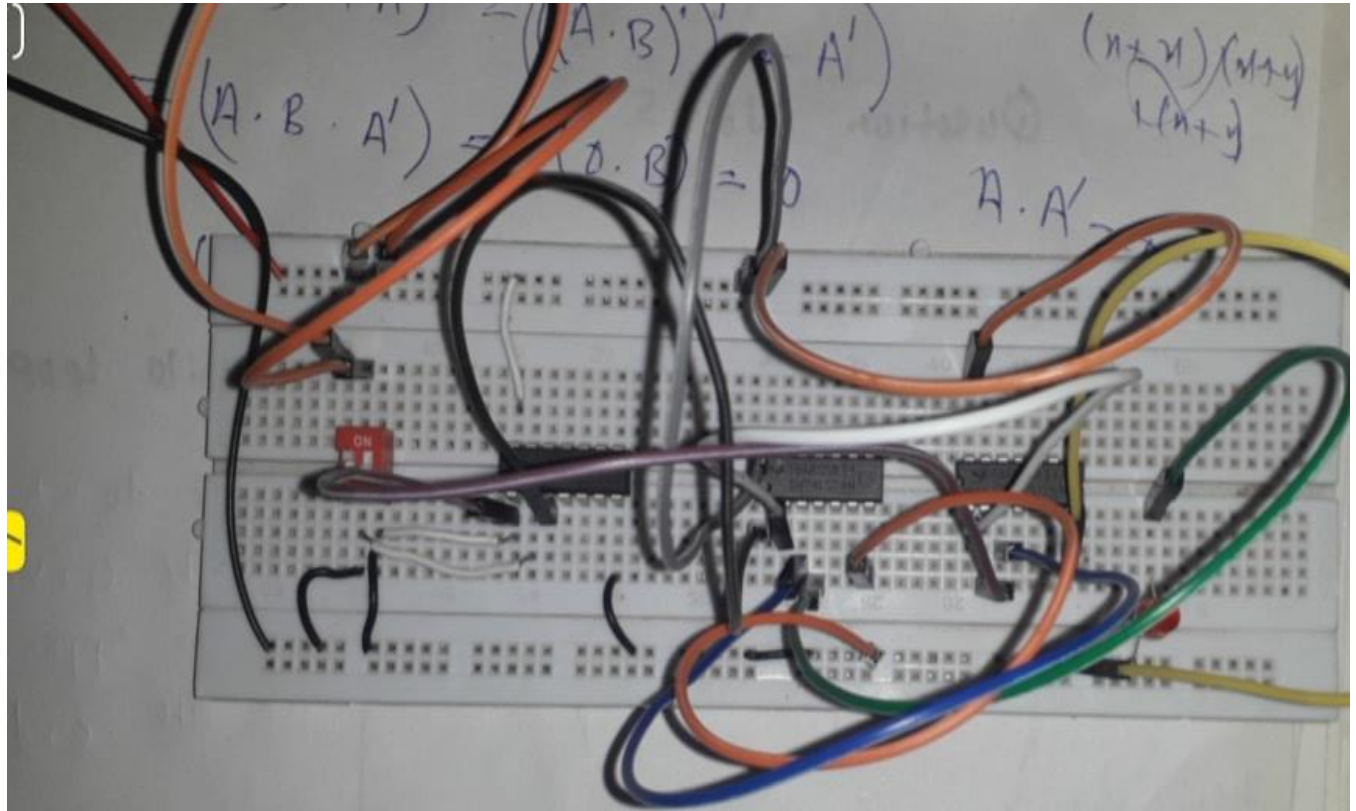


- Determine experimentally whether the given circuits are equivalent. Then use DeMorgan's theorem to prove your answer algebraically.

Experimental circuit:-

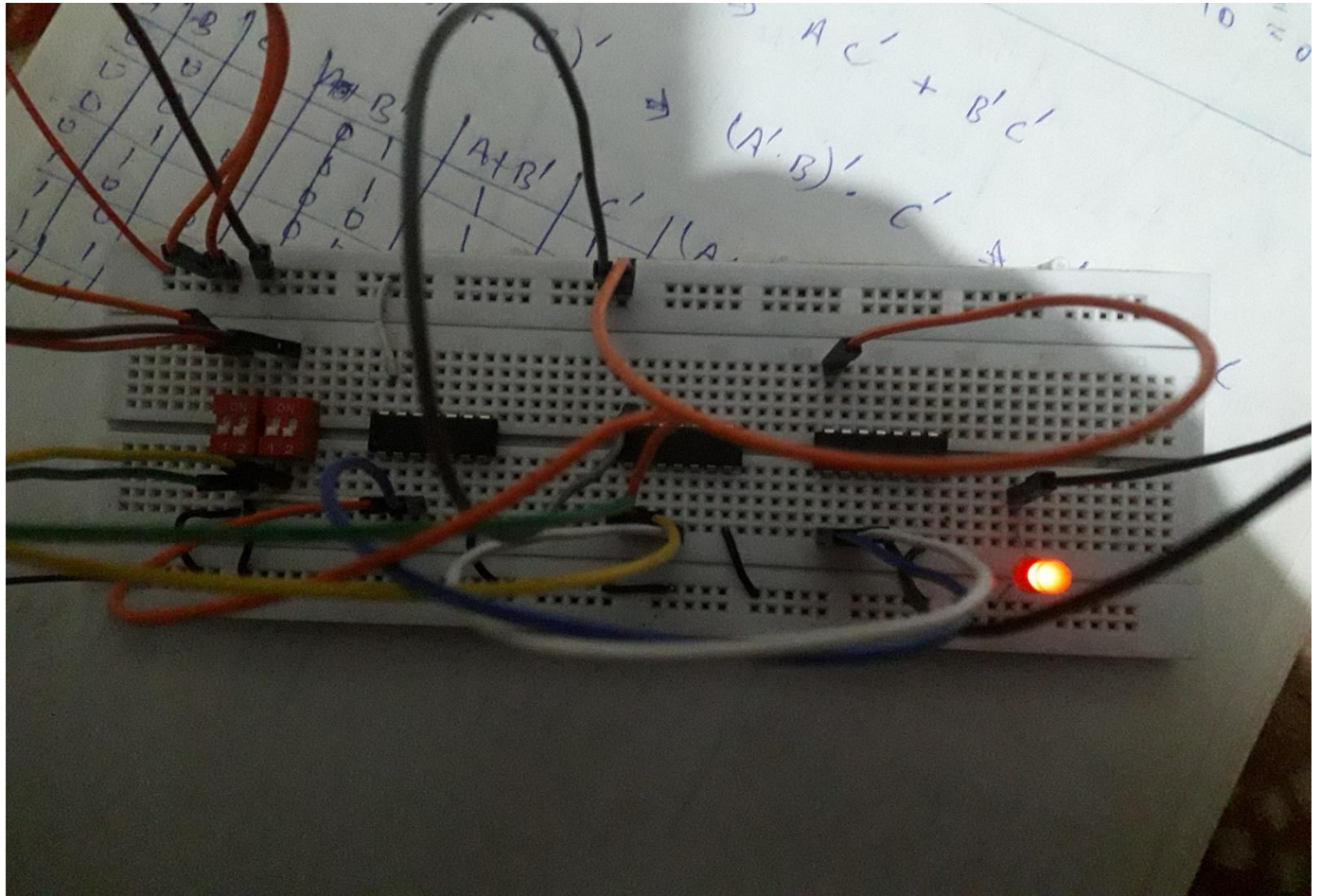


Expressions:-

1. $(A+B').C'$

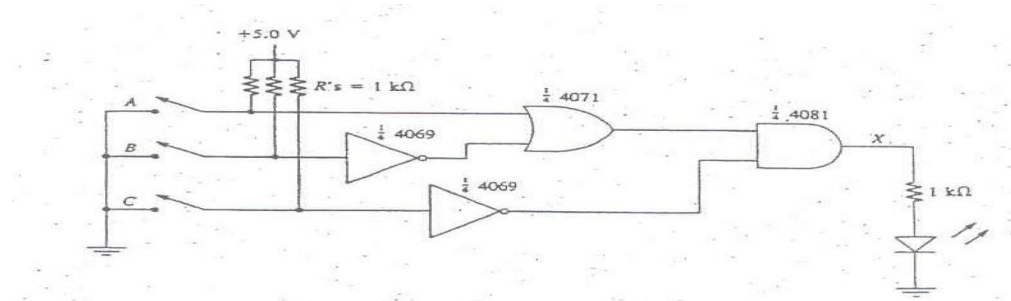

2. $((A'.B)+C)'$

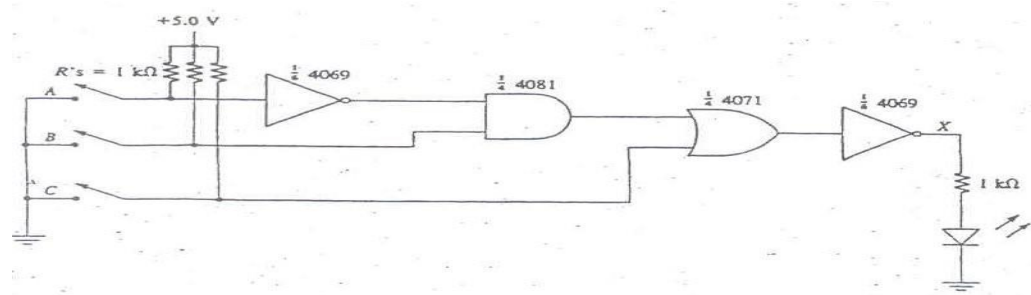

Algebraically:-

1st expression:-

$$(A+B').C' = A.C' + B'.C' \dots\dots\dots A$$

2nd expression:-

$$((A'.B)+C)' = (A'.B).C'$$

$$= A+B'.C'$$

$$((A'.B)+C)' = A.C' + B'.C' \dots\dots\dots B$$

Hence proved both equations are equals algebraically.